

### 3. Grouping of Resistors & Kirchhoff's Rule


#### 1. Grouping of resistances:

**(a) Series Grouping:** Supposed the resistances  $R_1$ ,  $R_2$  and  $R_3$  are grouped in series and a pd  $V$  is applied between  $A$  and  $B$ . Current through all the resistors will be the same. Let it be  $i$ .

The potential drop across different resistors are given by:  $V_1 = i_1 R_1$ ,  $V_2 = i_2 R_2$  and  $V_3 = i_3 R_3$ .

Therefore net potential drop across the combination (between  $A$  and  $B$ ) will be:

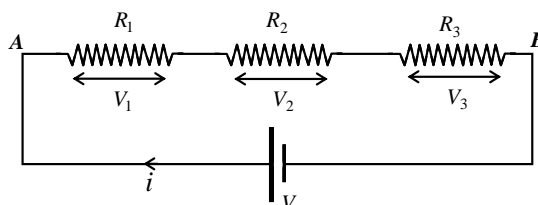
$$V = V_1 + V_2 + V_3 = i(R_1 + R_2 + R_3) \Rightarrow \frac{V}{i} = R_1 + R_2 + R_3.$$



Since  $V/i$  = equivalent resistance between  $A$  and  $B$ .  $\therefore \Rightarrow R_{eq} = R_1 + R_2 + R_3$

For  $n$  resistors in series,  $R_{eq} = \sum_{i=1}^n R_i$

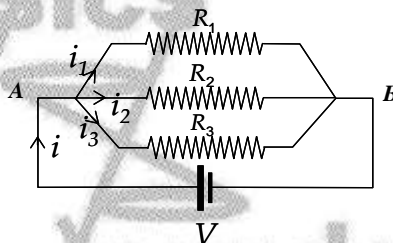**(b) Parallel Grouping:** Let there be resistances  $R_1$ ,  $R_2$ ,  $R_3$  grouped in parallel between  $A$  and  $B$  and pd applied across the combination is  $V$ .



Therefore, pd across each resistor is the same and equal to  $V$ , hence current through them will be different. If total current flowing through the grouping is  $i$  and supposed  $i_1$ ,  $i_2$ ,  $i_3$  are the currents through  $R_1$ ,  $R_2$ ,  $R_3$  respectively, then,

$$i = i_1 + i_2 + i_3 \Rightarrow i = V/R_1 + V/R_2 + V/R_3 \Rightarrow i/V = 1/R_1 + 1/R_2 + 1/R_3$$

Since  $\frac{i}{V} = \frac{1}{R_{eq}}$ , therefore,  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ .

For  $n$  resistors in parallel,  $\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_{eq}}$ .

#### 2. Kirchhoff's Rule.

**(a) Point- rule:** In a circuit, algebraic sum of total currents meeting at a point is zero.

Or, the sum of incoming currents = sum of outgoing currents.


This is based on charge conservation principle.

**Explanation:** According to charge conservation principle, no point in a circuit with steady current can be a source or a sink of charges. Therefore, total charge arriving at a point per second must be equal to those leaving the point.

In other words, net current arriving at a point is equal to the net current leaving that point.

For example, if currents  $i_1$ ,  $i_2$ ,  $i_3$ , arrive at a point and  $i_4$ ,  $i_5$  leave that point, then,
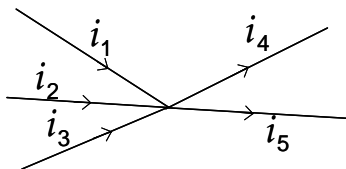
$$i_1 + i_2 + i_3 = i_4 + i_5. \text{ Or, } i_1 + i_2 + i_3 - i_4 - i_5 = 0.$$



## Chapter 3- Current Electricity


Taking incoming currents to be +ve, and outgoing currents to be -ve, the point rule can be generalised as :  $\sum i = 0$ .

**(b) Mesh or loop rule:** In a closed circuit, sum of the *potential drops* (current  $\times$  resistance) across the resistors is equal to the net *emf* inserted in the loop.

$$\Rightarrow \sum iR = \sum E.$$

This rule is based on the *energy conservation principle*.

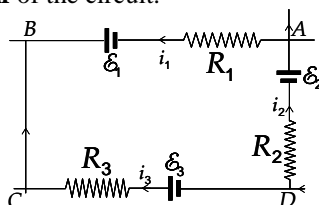**Explanation:** - Potential drop ( $iR$ ) represents total energy dissipated per unit charge flow in a resistor. Therefore the total potential drop represents total energy dissipated per unit charge in the circuit. By energy conservation principle, this must be equal to the energy supplied by the *emf seats* of the circuit per unit charge flow, i.e., the **net emf** of the circuit.



In the given mesh, taking the direction of current sent by  $E_1$  to be +ve, the net emf of the circuit is  $E_1 + E_3 - E_2$ , sending current anticlockwise.

Total potential drop while traversing the loop anticlockwise is  $i_1 R_1 - i_3 R_3 + i_2 R_2$ .

Hence by loop rule  $i_1 R_1 - i_3 R_3 + i_2 R_2 = E_1 - E_3 + E_2$ .

In general,  $\sum iR = \sum E$ .

**Note:** The Kirchhoff's loop rule can be stated alternatively as follows: **Sum of the potential drops across the resistors and emf seats in a closed loop is always zero.**


Starting from point A we have total potential drops,  $-i_1 R_1 + E_1 - E_3 + i_3 R_3 - i_2 R_2 + E_2 = 0$ .

Or,  $i_1 R_1 - i_3 R_3 + i_2 R_2 = E_1 - E_3 + E_2$ .
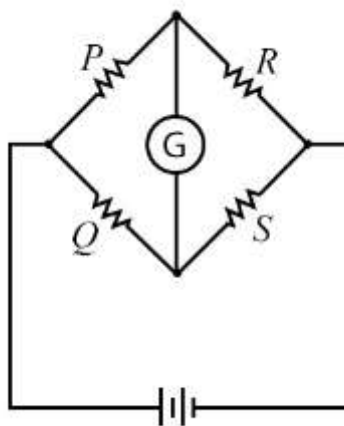
### 3. Wheatstone's bridge:

A four-resistance mesh used to measure unknown resistance is called a 'Wheatstone's bridge'.

**Construction:** It consists of four arms forming a rectangle, each containing a resistance. One pair of diagonal points is connected to emf terminals and the other to a galvanometer.



### 4. Deduction of balancing condition of a WSB:

Let total current  $i$  flows in to the Wheatstone's bridge.

According to junction rule, at points A, B, C and D:


At point A, if  $i_1$  flows through  $P$  then  $i - i_1$  will flow through  $Q$ .

At point C,  $i_1$  is divided into  $i_g$  and  $i_1 - i_g$ , which flows through the galvanometer (with resistance  $G$ ) and  $R$ , respectively.

At points D and B, currents combine, current through  $S$  is  $i - i_1 + i_g$  and current  $i$  emerges at B.

Applying Kirchhoff's mesh rule for loop ACDA,  $-i_1 P - i_g G + (i - i_1) Q = 0$ . ---- (i)

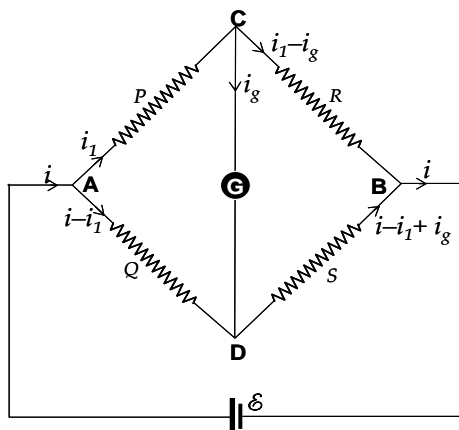For loop CDBC,  $-i_g G - (i - i_1 + i_g) S + (i_1 - i_g) R = 0$ . ----- (ii)



When the values of  $P$ ,  $Q$ ,  $R$  and  $S$  is so chosen that  $i_g = 0$ , the bridge is called '**balanced**'.

In this condition, the potentials of C and D are the same and equations (i) and (ii) take the form,

$$-i_1 P + (i - i_1) Q = 0 \quad \text{and} \quad -(i - i_1) S + i_1 R = 0$$

Solving them we have  $\boxed{\frac{P}{Q} = \frac{R}{S}}$ .

This is the **balancing condition** of WSB.