## 1. Capacitor:

*Capacitor*: An arrangement of conductors to store charge, hence electrical energy is called a 'capacitor'.

In practice, a capacitor consists of two conductors: one having charge and another earthed, separated by a small gap and filled with a dielectric (insulator). The system of these two conductors is called 'plates'.

The charged and the earthed plates have equal and opposite charges, therefore the net charge on a capacitor is zero.

## 2. Capacitance of a Capacitor:

*Capacitance of a Capacitor:* Capacitance of a capacitor is the ratio of the charge on the +ve plate of the capacitor and potential difference between the plates.

$$\Rightarrow C = \frac{q}{V_{Plates}}.$$

Dependence of capacitance: Capacitance of a capacitor depends upon:

(i) Plates area A, (ii) Separation between the plates d and (iii) d.e.c. of the medium between the plates k, i.e.



# 3. Deduction of capacitance of parallel plate capacitor:



Two parallel plates of area A are arranged at a separation d.

Field between the plates is uniform and equal to  $E = \frac{\sigma}{\epsilon_0}$ .

- $\therefore$  Potential difference between the plates V = Ed.
- $\Rightarrow V = \frac{\sigma}{\varepsilon_0} d = \frac{q}{A\varepsilon_0} d$ , where q is the total charge on the charged plate.
- $\therefore \text{ Capacitance } C = \frac{q}{V} = q / \frac{qd}{\varepsilon_0 A} \, . \, \left| \Rightarrow C = \frac{\varepsilon_0 A}{d} \right|.$

When an insulator of d.e.c. *k* is filled between the plates then  $C = \frac{\varepsilon_0 kA}{c}$ 

#### 4. Grouping of a capacitor:

A combination of different capacitor is equivalent to a single capacitor. This is called a grouping. The simplest groupings are (i) series and (ii) parallel.

(a) Series grouping: When capacitors are grouped with alternate plates joined with one another, the grouping is called *series*. In such a connection, the charge on each capacitor is the same.

Let it be q. But p.d. across each capacitors will be different, let them be  $V_1$ ,  $V_2$ ,  $V_3$  across  $C_1$ ,  $C_2$ ,  $C_3$ 

respectively. 
$$\therefore V_1 = \frac{q}{C_1}$$
,  $V_2 = \frac{q}{C_2}$ , and  $V_3 = \frac{q}{C_3}$ .



Total potential difference across combination is V, then,

$$V = V_1 + V_2 + V_3 = q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) \implies \frac{V}{q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$

Since q is total charge of the combination and V is pd across the combination, therefore q/V = C is the equivalent capacitance of the combination.

: Equivalent capacitance of series combination of capacitors 
$$C_1$$
,  $C_2$ ,  $C_3$  is  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ 

In general the equivalent capacitance  $\frac{1}{C} = \sum_{n} \frac{1}{C_i}$ , for *n* capacitors.

(b) **Parallel combination**: If charged plates of all capacitors are joined to one common point and earthed plates to another common point, the combination is called *parallel*.

If  $C_1$ ,  $C_2$  and  $C_3$  are capacitors joined in parallel then potential difference across each is the same. Let it be V. Let charges on them be  $Q_1$ ,  $Q_2$ , and  $Q_3$  respectively, then  $Q_1 = C_1V$ ,  $Q_2 = C_2V$  and  $Q_3 = C_3V$ .

 $\therefore \text{ Net charge on combination } Q = Q_1 + Q_2 + Q_3, \implies Q = V(C_1 + C_2 + C_3). \implies \frac{Q}{V} = C_1 + C_2 + C_3.$ 

Since Q/V = C is the equivalent capacitance of the combination, therefore,  $C = C_1 + C_2 + C_3$ 



5. Capacitors with mixed dielectrics:



(i) If dielectrics of d.e.c.  $k_1$ ,  $k_2$  and  $k_3$  are arranged in full area of the plates with partial widths  $d_1$ ,  $d_2$  and  $d_3$ , the arrangement is series combination of three capacitors of capacitances  $C_1 = \frac{k_1 \varepsilon_0 A}{d_2}$ ,

$$C_2 = \frac{k_2 \varepsilon_0 A}{d_2} \text{ and } C_3 = \frac{k_3 \varepsilon_0 A}{d_3}. \text{ Hence equivalent capacitance is } \frac{1}{C_{eq}} = \frac{1}{\varepsilon_0 A} \left( \frac{d_1}{k_1} + \frac{d_2}{k_2} + \frac{d_3}{k_3} \right).$$

Equivalent dielectric constant:  $C_{eq} = \frac{\varepsilon_0 A}{d\left(\frac{d_1}{k_1 d} + \frac{d_2}{k_2 d} + \frac{d_3}{k_3 d}\right)}$ .

Therefore the equivalent dielectric constant,  $\frac{1}{k_{eq}} = \frac{d_1}{k_1 d} + \frac{d_2}{k_2 d} + \frac{d_3}{k_3 d}$ .

> If  $d_1 = d_2 = d_3 = d/3$  then  $\frac{1}{k_{eq}} = \frac{1}{3} \left( \frac{1}{k_1} + \frac{1}{k_2} + \frac{1}{k_3} \right).$ 

>If there are only two dielectrics then  $\frac{1}{k_{eq}} = \frac{1}{2} \left( \frac{1}{k_1} + \frac{1}{k_2} \right)$ , or,  $k_{eq} = \frac{2k_1k_2}{k_1 + k_2}$ . (Fig.1)

(ii) If dielectrics are arranged in full width and in partial plate areas  $A_1$ ,  $A_2$  and  $A_3$ , then the arrangement is a parallel combination of three capacitors of capacitances are:

$$C_1 = \frac{k_1 \varepsilon_0 A_1}{d}$$
,  $C_2 = \frac{k_2 \varepsilon_0 A_2}{d}$  and  $C_3 = \frac{k_3 \varepsilon_0 A_3}{d}$ .

Hence equivalent capacitance is  $C_{eq} = \frac{\varepsilon_0}{d} (k_1 A_1 + k_2 A_2 + k_3 A_3).$ 

**Equivalent dielectric constant:**  $C_{eq} = \frac{\varepsilon_0 A}{d} \left( \frac{k_1 A_1 + k_2 A_2 + k_3 A_3}{A} \right).$ 

Therefore equivalent dielectric constant,  $k_{eq} = \frac{k_1 A_1 + k_2 A_2 + k_3 A_3}{A}$ .

▶ If 
$$A_1 = A_2 = A_3 = A/3$$
 then.  $k_{eq} = \frac{k_1 + k_2 + k_3}{3}$ 

► If there are only two dielectrics then  $k_{eq} = \frac{k_1 + k_2}{2}$ . (Fig. 2)



(iii) This is a special case of (i). The capacitor is the combination of an air capacitor of separation d-t and another of t with dielectric k.

Hence 
$$\frac{1}{C_{eq}} = \frac{1}{\varepsilon_0 A} \left( \frac{d-t}{1} + \frac{t}{k} \right)$$
.  $\Rightarrow C_{eq} = \frac{\varepsilon_0 A}{\left( d-t + \frac{t}{k} \right)} = \frac{k\varepsilon_0 A}{k d-t (k-1)}$ .  
Equivalent dielectric constant:  $C_{eq} = \frac{k\varepsilon_0 A}{d\left( k - \frac{t(k-1)}{d} \right)}$ .

Therefore equivalent dielectric constant, 
$$k_{eq} = \frac{k}{\left(k - \frac{t(k-1)}{d}\right)}$$
.

> If 
$$t = d/2$$
 then.  $k_{eq} = \frac{2k}{k+1}$ .

## 6. Energy stored in a charged capacitor:

Let a capacitor be charged to a charge q and potential difference between the plates is V. If capacitance is C then  $V = \frac{q}{C}$ . Work done in transferring a further dq charge on the +ve plate from the negative plate,  $dW = Vdq = \frac{qdq}{C}$ .

:. Total work done in depositing a total of charge Q on the +ve plate  $w = \int_{0}^{Q} dw$ .

$$\Rightarrow W = \int_{0}^{Q} \frac{q dq}{C} = \frac{1}{C} \left[ \frac{q^2}{2} \right]_{0}^{Q} \Rightarrow W = \frac{Q^2}{2C}.$$

This work done is stored in the capacitor as potential energy in the electric field between the plates.

Therefore potential energy of the capacitor is  $U = \frac{Q^2}{2C}$  or  $U = \frac{1}{2}CV^2$  or  $U = \frac{1}{2}QV$ .

# 7. Energy density of an electric field:

Energy stored in a parallel plate capacitor is given by the formula  $U = \frac{1}{2}CV^2$ .

This energy is stored in the electric field between the plates of a capacitor.

Considering the capacitor to be a parallel plate capacitor,  $U = \frac{1}{2} \frac{\varepsilon_0 A}{d} V^2 = \frac{1}{2} \varepsilon_0 \frac{V^2}{d^2} A d$ .

 $\frac{V}{d}$  is the uniform field *E* between the plates and *Ad* is the volume of the space between the plates in which uniform field exists.

Therefore,  $\frac{U}{Ad} = \frac{1}{2}\varepsilon_0 E^2$ , where  $\frac{U}{Ad} = u$  = energy per unit volume in the field is called energy density

of the field. Therefore the expression for the electric field energy is  $u = \frac{1}{2} \varepsilon_0 E^2$ .

This result is valid for a non-uniform electric field also. At a point where electric field is E the energy density will be  $u = \frac{1}{2} \varepsilon_0 E^2$ .

### 8. Energy loss in charging of capacitor:

Let a charge q be stored on a capacitor. Hence work done by the battery W = qV, where V is the pd between the terminals of the battery and battery is assumed to be ideal. Therefore energy supplied by

the battery 
$$U_{battery} = qV = CV^2$$
. Energy stored in the capacitor  $U_{stored} = \frac{CV^2}{2}$ 

Therefore, half part of the energy supplied is lost in instantaneous current flowing through the circuit during the charging process.

## 9. Energy loss in reconnection of two charged capacitors:

Supposed that two capacitors  $C_1$  and  $C_2$  are initially charged to pds  $V_1$  and  $V_2$ .

Initial energy  $U_i = \frac{1}{2}C_1V_1^2 + \frac{1}{2}C_2V_2^2$ .

They are connected in parallel. Supposed across the combination the pd = V.

Therefore 
$$\frac{q_1}{C_1} = \frac{q_2}{C_2} = V$$
.  $\Rightarrow V = \frac{(q_1 + q_2)}{C_1 + C_2}$ .  $(q_1 + q_2)$  is the total initial charge  $C_1V_1 + C_2V_2$ .

Therefore  $V = \frac{(C_1V_1 + C_2V_2)}{C_1 + C_2}$ . Now final energy  $U_f = \frac{1}{2}(C_1 + C_2)V^2 = \frac{(C_1V_1 + C_2V_2)^2}{2(C_1 + C_2)}$ .

Therefore, change in energy,

$$U_i - U_f = \frac{1}{2} \left( C_1 V_1^2 + C_2 V_2^2 \right) - \frac{\left( C_1 V_1 + C_2 V_2 \right)^2}{2 \left( C_1 + C_2 \right)} \Rightarrow U_i - U_f = \frac{C_1 C_2}{2 \left( C_1 + C_2 \right)} \left( V_1 - V_2 \right)^2 > 0. \implies U_i > U_f.$$

Special case: If two capacitors are connected with reversed polarity then energy loss is:

$$U_i - U_f = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 + V_2)^2$$
. That is loss is greater

10. Changes taking place when a dielectric slab is inserted between the plates of a parallel plate capacitor: (i) When plates are connected to a battery, (ii) when plates are charged but not connected to a battery:

(i) When plates are connected to a battery, and a dielectric slab is inserted between the plates of the capacitor then:

A. PD between the plates, hence the electric field between the plates remains constant.

**B.** Capacitance of the capacitor changes (increases) k times, where k is the dielectric constant of the capacitor.

C. Charge is directly proportional to the capacitance hence the charge also increases k times. That is new charge on the capacitor is Q' = kQ.

Therefore the charge increment is  $\Delta Q = (k-1)Q$ .

**D**. Induced charge on the surfaces of the dielectric is  $Q_i = Q_{free}(1-\frac{1}{L})$ .

$$\Rightarrow Q_i = kQ(1 - \frac{1}{k}) = (k-1)Q = CV(k-1)Q$$

**E.** Since the energy is proportional to the capacitance then energy also increases k times.  $U = \frac{1}{2} kCV^2$ .

(ii) If capacitor is charged and the cell is not connected and a dielectric slab is inserted between the plates of the capacitor then

A. Net charge on the capacitor remains the same.

**B**. Capacitance increases *k* times.

**C.** Field between the plates of the capacitor becomes 1/k times. As a result the potential difference between the plates also decreases 1/k times. V' = V/k.

**D.** Since energy of the capacitor is inversely proportional to the capacitance therefore the energy deceases 1/k times.  $U' = \frac{1}{2} kC(V/k)^2 \Rightarrow U' = \frac{1}{2} CV^2/k$ .

E. Since net charge on the capacitor remains the same, the induced charge on the dielectric surfaces is

$$Q_i = Q \left(1 - \frac{1}{k}\right) \,.$$